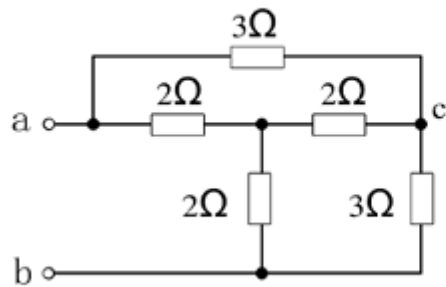


(homework 1)

2.2 For the circuits in fig2.2, obtain the equivalent resistance at terminals a-b by wye-Delta transformations


2.2 用电阻的 γ - Δ 的等效变换求题2.2图所示电路的等效电阻。



题2.2图

2.9 Use mesh analysis to obtain I and U in the circuit in fig2.9


2.9 用网孔电流法求题2.9图中的电流 I 和电压 U 。

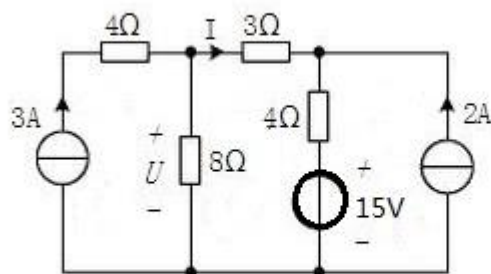

题2.9图

2.10 Use Nodal analysis to obtain I_1 I_2 I_3 in the circuit in fig2.10


2.10 用结点电压法求题2.10图中各支路电流。

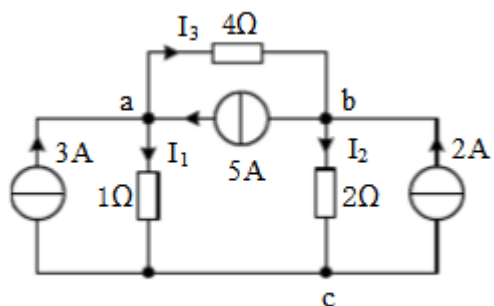

题2.10图

2.11 Use Nodal analysis to obtain U_a U_b U_c in the circuit in fig2.10


2.11 用结点电压法求题 2.11 图所示电路各结点电压。

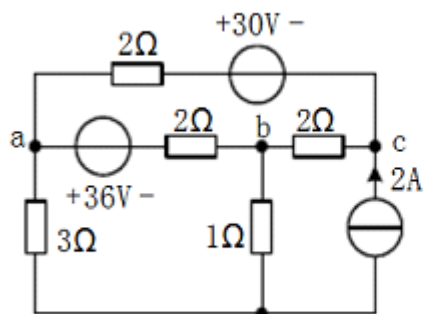

题2.11图

2.14 Please calculate U by the “superposition law”

2.14 利用叠加定理求题2.14图所示电路中电流源上的电压 U 。

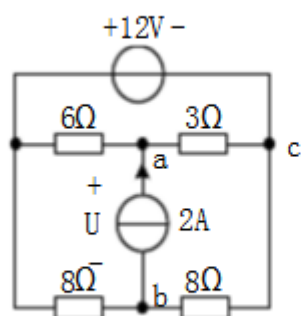


题2.14图

2.22 & 2.23


Find the Thevenin equivalent at terminals a-b of the circuit in Fig2.22 & Fig2.23

2.22 求题2.22图所示电路的戴维南等效电路。

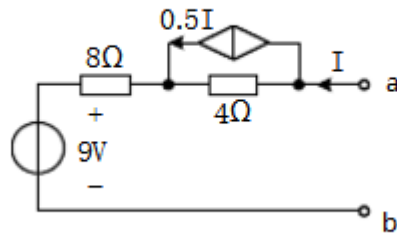

题2.22图

2.23 求题2.23图所示电路的戴维南等效电路。

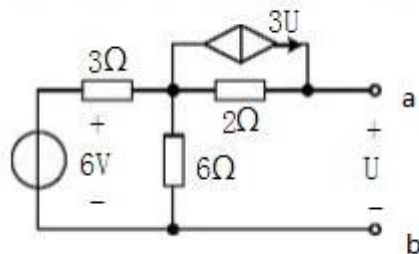

题2.23图